

CBCS SCHEME

USN 2 2 8 1 8 C 2 0 1 2

18ELN14/24

First/Second Semester B.E. Degree Examination, June/July 2019 Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. What is semiconductor diode? Explain the different equivalent circuits of diode. (06 Marks)
- b. Explain the working of photodiode. (05 Marks)
- c. With a neat circuit diagram and waveforms, explain the working of full wave bridge rectifier. Also derive V_{dc} and V_{rms} values for full wave rectifier. (09 Marks)

OR

- 2 a. A full wave rectifier uses 2 diodes having internal resistance of 20Ω each. The transformer rms secondary voltage from centre to each end is 50V. Find I_m , I_{dc} , I_{rms} and V_{dc} if the load is 980Ω . (06 Marks)
- b. Explain the functional block diagram of $78xx$ series voltage regulator. (06 Marks)
- c. Explain how Zener diode can be used as a voltage regulator. Give detail mathematical analysis. (08 Marks)

Module-2

- 3 a. With a neat circuit diagram explain the working of CMOS inverter. (06 Marks)
- b. For a N-channel JFET if $I_{DSS} = 8mA$ and $V_p = -5V$, calculate I_D at $V_{as} = -3V$ and V_{as} at $I_D = 3mA$. (05 Marks)
- c. Explain the construction, working and characteristics of N- channel JFET. (09 Marks)

OR

- 4 a. Explain the working of SCR using two transistor model. (06 Marks)
- b. What is commutation in SCR? Explain two types of commutation. (05 Marks)
- c. Explain the construction, working and characteristics of enhancement type MOSFET. (09 Marks)

Module-3

- 5 a. What is Op - AMP? List the characteristics of ideal Op - Amp. (06 Marks)
- b. Explain how Op - Amp can be used as i) Integrator ii) Voltage Follower. (08 Marks)
- c. Find the output of the Op - Amp circuit shown in Fig Q5(c) below

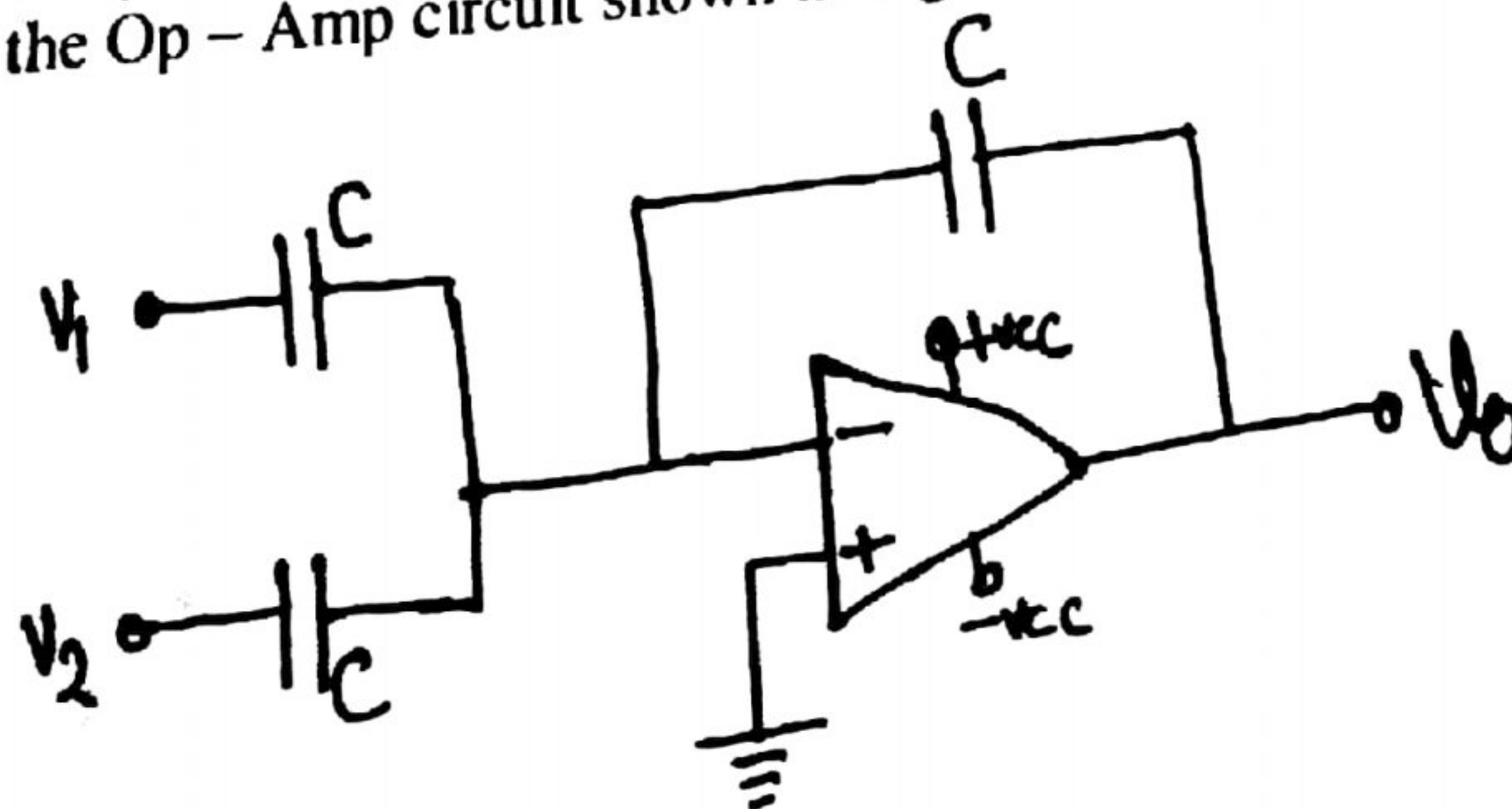


Fig Q5(c)

(06 Marks)

OR

- 6 a. Explain the following terms with respect to Op - Amp
 i) CMRR ii) Slew Rate iii) Output offset voltage iv) Supply voltage Rejection Ratio (08 Marks)
 b. Design an Op - Amp circuit to obtain output expression as $V_0 = -[V_1 + 3V_2 + 5V_3]$. (06 Marks)
 c. Explain how Op - Amp can be used as differentiator. (06 Marks)

Module-4

- 7 a. What is feedback amplifier? What are the properties of negative feedback amplifier? (06 Marks)
 b. Explain how transistor can be used as an amplifier. (06 Marks)
 c. With a neat circuit diagram and waveforms, explain the working of 555 timers as an oscillator. (08 Marks)

OR

- 8 a. Draw the block diagram of voltage series negative feedback amplifier and derive the expression for its voltage gain. (06 Marks)
 b. Design a RC phase shift oscillator for a frequency of 1KHz. Draw the circuit diagram with designed values. (06 Marks)
 c. With a neat circuit diagram, explain the working of Wein Bridge oscillator. (08 Marks)

Module-5

- 9 a. Perform the following :
 i) Convert $(925.75)_{10}$ to base - 2 and base - 16
 ii) Subtract from $(11011.11)_2$ from $(10101.11)_2$ using 2's complement method. (06 Marks)
 (15) b. With a block diagram explain the working of 3-bit asynchronous counter. (06 Marks)
 (16) (11) c. What is multiplexer? Implement 8:1 multiplexer using basic gates. (08 Marks)

OR

- 10 a. Simplify $S = A \oplus B \oplus C$ and realize using basic gates. - L3 (02) (05 Marks)
 b. What is flip-flop? Explain the operation of master slave JK flip flop. (06 Marks)
 c. Implement full adder using two half adders. (16) (04 Marks)
 d. With a block diagram, explain the working of basic communication system. (05 Marks)
 (15)

GBGS Scheme

USN

--	--	--	--	--	--	--	--	--	--

17ELN15

First Semester B.E. Degree Examination, Dec. 2017/Jan. 2018

Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Explain the operation of PN junction diode under forward and reverse biased conditions. (06 Marks)
with the help of VI characteristics curve.
- b. Derive the relation between α and β . Calculate I_C and I_E for transistor that has $\alpha_{dc} = 0.98$ and $I_B = 100 \mu A$. (06 Marks)
- c. With a neat circuit diagram and waveforms, explain the working of centre-tap full wave rectifier and derive the efficiency for the same. (08 Marks)

OR

- 2 a. With a neat diagram, explain the operation of PNP and NPN transistor. (08 Marks)
- b. A half wave rectifier from a supply 230 V 50 Hz with step down transformer ratio 3:1 to a resistive load of $10 K\Omega$. The diode forward resistance is 75Ω and transformer secondary is 10Ω . Calculate the DC current, DC voltage, efficiency and ripple factor. (06 Marks)
- c. With neat circuit diagram, explain the common emitter circuit and sketch the input and output characteristics. (06 Marks)

Module-2

- 3 a. With a necessary equation and circuit, explain the base-bias transistor circuits. (06 Marks)
- b. Design an Adder using op-amp to give the output voltage ,
 $V_o = -[2V_1 + 3V_2 + 5V_3]$ (06 Marks)
- c. Derive the equations for output voltage for an inverting amplifier and an integrator. (08 Marks)

OR

- 4 a. Explain the characteristics of an ideal op-amp. Mention the applications. (06 Marks)
- b. Accurately analyze the voltage divider bias which has $V_{CC} = 18 V$, $R_1 = 33 K\Omega$, $R_2 = 12 K\Omega$ and $R_E = 1 K\Omega$. Determine V_E , V_C , V_{CE} , I_C and Q point, when transistor $h_{FE} = 200$. (08 Marks)
- c. Write short notes on op-amp virtual ground concept. (06 Marks)

Module-3

- 5 a. Perform the following:
 - i) Convert $(57345)_{10} = (\quad)_{16}$
 - ii) Subtract $(28)_{10} - (19)_{10}$ using 2's complement method. (06 Marks)
- b. Realize $Y = AB + CD + E$ using NAND gate. (06 Marks)
- c. Explain the full adder circuit with truth table. Realize the circuit for sum and carry using logic gates. (08 Marks)

OR

- 6 a. Perform the following:
- i) Convert $(FA27D)_{16} = ()_2 \rightarrow = ()_8 = ()_{10}$
 - ii) Subtract $10.0101 - 101.1110$ using 1's complement method.
- b. $Y = A + \bar{A}B + ABC$ simplify and implement using logic gates and NOR gates.
- c. State and prove De Morgan's theorem using two variable.

(06 Marks)

(06 Marks)

(08 Marks)

(04 Marks)

(06 Marks)

(10 Marks)

- 7 a. Bring out differences between flip flops and latches.
- b. Explain SR flipflop with circuit diagram and truth table.
- c. With a neat block diagram explain the architecture of 8051 microcontroller.

OR

- 8 a. Explain the operation of NAND gate latch with circuit and truth table.
- b. What is stepper motor? With a neat block diagram, explain the working principle of microcontroller based stepper motor control system.

(10 Marks)

(10 Marks)

Module-5

- 9 a. Define communication. With neat block diagram, explain the elements of communication system.
- b. Derive an expression for amplitude modulation and draw the necessary waveforms.
- c. What is transducer? Compare the active and passive transducers.

(06 Marks)

(08 Marks)

(06 Marks)

OR

- 10 a. Bring out the difference between amplitude modulation and frequency modulation.
- b. If a FM wave represented by the equation $V = 10\sin(8 \times 10^8 + 4\sin 1000t)$, calculate:
- i) Carrier frequency
 - ii) Modulating frequency
 - iii) Modulation index
 - iv) Band width
- c. With necessary diagram and equations, explain the following:
- i) Piezo-electric transducer
 - ii) LVDT.

(06 Marks)

(06 Marks)

(08 Marks)

Danish Kumar

USN

2 V S 1 6 E C 0 0 7

CBCS Scheme

15ELN15/25

First/Second Semester B.E. Degree Examination, June/July 2017
Basic Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

- 1
- Module-1**
- a. Explain briefly the PN junction diode characteristics. (06 Marks)
 - b. Explain Zener diode voltage regulator circuit with no load and with load. (06 Marks)
 - c. Derive the relationship between α and β . Calculate the value of I_c for a transistor that has $\alpha = 0.98$ and $I_b = 200 \mu A$. (04 Marks)

- 2
- OR**
- a. Explain briefly the common emitter circuit and sketch the input and output characteristics. Also explain operating regions by indicating them on characteristics curve. (06 Marks)
 - b. With a neat circuit diagram and waveforms, explain the working of a half-wave rectifier. (06 Marks)
 - c. Explain briefly capacitor filter circuit. (04 Marks)

- 3
- Module-2**
- a. What is a DC load line? Explain the voltage divider bias circuit. (08 Marks)
 - b. Mention and explain the characteristics of ideal operational amplifier. (04 Marks)
 - c. Derive the expression of integrator with circuit diagram. (04 Marks)

- 4
- OR**
- a. With neat circuit and necessary equations, explain the voltage follower. (06 Marks)
 - b. Explain the base bias circuit. (04 Marks)
 - c. Explain briefly inverting and non-inverting operational amplifiers. (06 Marks)

- 5
- Module-3**
- a. State and prove De-Morgan's theorem with truth table. (06 Marks)
 - b. Explain the basic gates AND, OR and NOT gates with truth tables. (06 Marks)
 - c. Explain the half-adder circuit. *using NAND gates* (04 Marks)

- 6
- OR**
- a. Explain the full-adder circuit. ✓ (06 Marks)
 - b. Simplify the given Boolean equation $Y = (A + \bar{B})(CD + E)$ and realize using NAND gates only. (04 Marks)
 - c. Convert the following:
 - i) $(49.5)_{10} = (?)_{16}$
 - ii) $(1062.403)_8 = (?)_{10}$
 - iii) $(642.71)_8 = (?)_2$(06 Marks)

- 7
- Module-4**
- a. What is R-S flip-flop? Explain its circuit diagram, logic symbol and truth table. (08 Marks)
 - b. Explain the architecture of 8051 microcontroller in detail. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. $42+8=50$, will be treated as malpractice.

15F1

OR

(08 Marks)
(08 Marks)

- 8 a. Explain the gated R-S flip-flop and clocked R-S flip-flop.
b. With the help of block diagram, explain the micro-controller based stepper motor control system.

Module-5

(06 Marks)
(06 Marks)
(04 Marks)

- 9 a. Explain the construction of LVDT and its operation.
b. Explain the frequency modulation with neat waveforms.
c. Explain with diagram the AM detection (demodulation).

OR

- 10 a. Explain the piezoelectric transducer and photoelectric transducer.
b. Explain with block diagram elements of communication system.
c. Compare AM and FM modulation.

(06 Marks)
(06 Marks)
(04 Marks)

* * * * *

18ELN14/24

Visvesvaraya Technological University, Belagavi

MODEL QUESTION PAPER


1st/2nd Semester, B.E (CBCS 2018-19 Scheme)

Course: 18ELN14/24- BASIC ELECTRONICS - Set no. 1

Time: 3 Hours

Max. Marks: 100

Note: (i) Answer Five full questions selecting any one full question from each Module.
(ii) Question on a topic of a Module may appear in either its 1st or/and 2nd question.

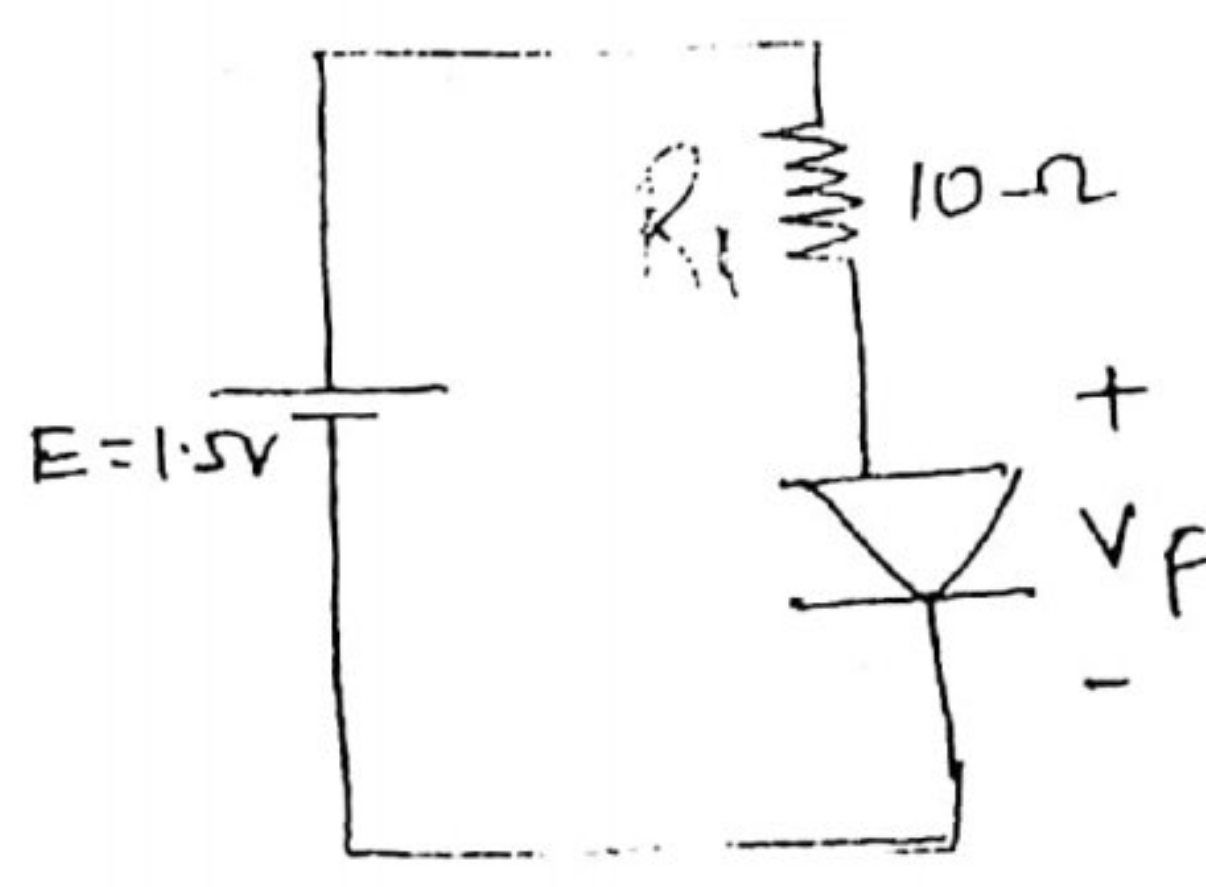Module-1			Marks
1	a	Explain the operation of p-n junction diode under forward and reverse biased condition	3
	b	Explain how Zener diode can be used as a voltage regulator	6
	c	A diode circuit shown below has $E=1.5V$, $R=10\text{ ohm}$. By assuming $V_f=0.7V$, calculate I_f for i) $r_d = 0$ ii) $r_d = 0.25\text{ ohm}$	6
			
Fig.Q.1(c)			
OR			
2	a	With a neat circuit diagram and waveform, explain the working of half-wave rectifier and derive the expression for average load current.	8
	b	Explain briefly the operation of a capacitor filter circuit.	1
	c	Explain the operation of 7805 fixed IC voltage regulator.	
Module-2			

- 3 a Explain the characteristics of N-channel JFET.
- b For E-MOSFET, determine value of I_D , if $I_{D(ON)} = 4\text{mA}$, $V_{gs(ON)} = 6\text{V}$, $V_T = 4\text{V}$ and $V_{gs} = 8\text{V}$.
- c Explain the construction and working of N-channel enhancement type MOSFET.

OR

- 4 a Draw and explain the operations of SCR using 2-transistor equivalent circuit.
- b Explain phase controlled application of SCR.
- c Explain the operation of a CMOS inverter.

Module-3

- 5 a For an op-amp (i) List the characteristics of an ideal op-amp and (ii) Draw the three input inverting summer circuit and derive an expression for its output voltage. ✓

b Define the terms

- i) Slew rate
ii) CMRR
iii) Common mode gain A_c of op-amp

- c Design an adder circuit using an op-amp to obtain an output voltage of $V_o = -[2V_1 + 3V_2 + 5V_3]$

OR

- 6 a Draw the working of an inverting op-amp. Derive the expression for its voltage gain. ✓

- b With a neat diagram, explain how an op-amp can be used as a differentiator.

- c Find the output V_o of following op-amp circuit.

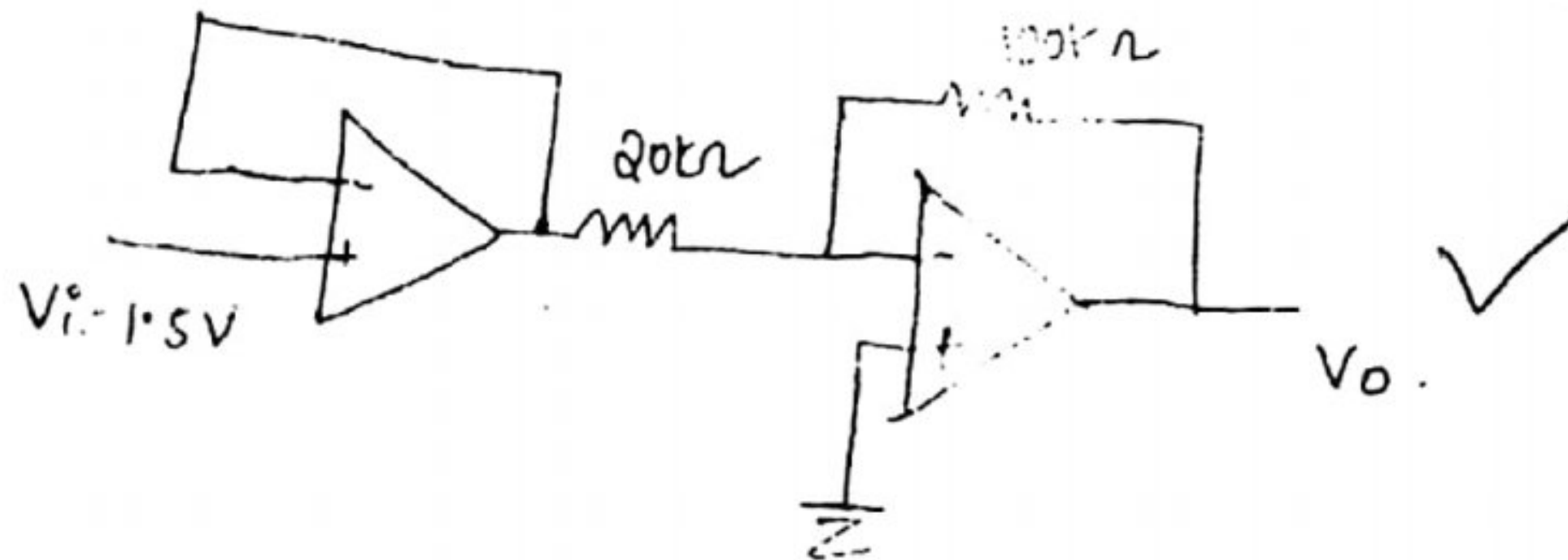


Fig. Q.6(c)